



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

Faculty of
Electrical
Engineering

CAD with HDL (SKEL 4273)

Section 1

“7-Tap FIR Filter”

Lecturer's Name:

Mdm Norlina Binti Paraman

Name	Matric No.	IC No.
Hong Sing Min	A12KE0149	920707-13-5390
Low Chea Seng	A12KE0162	921114-01-5099

Table of Content


No	Content	Page No
1.	Front cover	1
2.	Table of content	2
3.	Objective	3
4.	Introduction	3
	I. ASM Chart	4
	II. RTL Code	5
	III. Datapath Unit (DU) Design	5-8
	a. Functional Block Diagram	5
	b. Verilog HDL Coding	6-8
	IV. Control Unit (CU) Design	8-9
	a. RTL-CS Table	8
	b. Functional Block Diagram	8
	c. Verilog HDL Coding	9
	V. CU-DU Integration	10-11
	a. Top-Level Functional Block Diagram	10
	b. Top-Level Verilog HDL Coding	11
1	VI. Design Simulation	12-14
	a. Datapath Unit (DU)	12
	b. Control Unit (CU)	13
	c. CU-DU Integration	14
5.	Discussion	15
6.	Conclusion	15

OBJECTIVE

 1. To design a 7-tap FIR filter using RTL Design Methodology.

INTRODUCTION

Finite impulse response (FIR) filters are digital filters with finite impulse response. They are also known as non-recursive digital filters as they do not have feedback.



For a causal discrete-time FIR filter of order N , each value of the output sequence is a weighted sum of the most recent input values:

$$h[n] = \sum_{i=0}^N b_i \cdot \delta[n - i]$$

$$= \begin{cases} b_n & 0 \leq n \leq N \\ 0 & \text{otherwise} \end{cases}$$

$$y[n] = h[n] * x[n]$$

$$= b_0 x[n] + b_1 x[n - 1] + \dots + b_N x[n - N]$$

$$= \sum_{i=0}^N b_i \cdot x[n - i]$$

where:

- $x[n]$ is the input signal,
- $h[n]$ is the impulse response,
- $y[n]$ is the output signal,
- N is the filter order; an N th-order filter has $(N + 1)$ terms on the right-hand side
- b_i is the value of the impulse response at the i 'th instant for $0 \leq i \leq N$ of an N th-order FIR filter. If the filter is a direct form FIR filter then b_i is also a coefficient of the filter.

This computation is also known as discrete convolution.

The $x[n - i]$ in these terms are commonly referred to as *taps*, based on the structure of a tapped delay line that in many implementations or block diagrams provides the delayed inputs to the multiplication operations.

For our project, we are required to design a 7-tap FIR filter, which is of 6th order.

The impulse response of the filter as defined is nonzero over a finite duration.


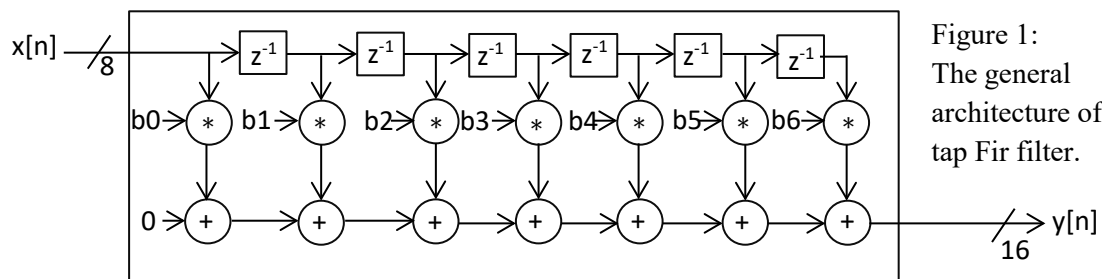


Figure 1:
The general
architecture of 7-
tap Fir filter.

I. ASM Chart

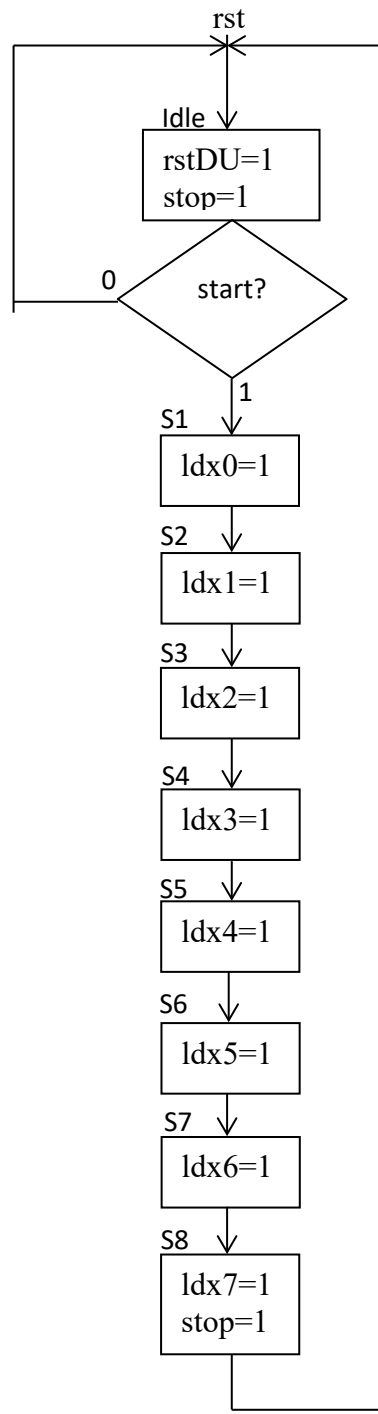


II. RTL Code

Idle:	$q \leftarrow 0;$ $stop = 0;$ (start)/ go to S1; (!start)/ go to Idle;
S1:	$q0 \leftarrow x0;$
S2:	$q1 \leftarrow x1;$
S3:	$q2 \leftarrow x2;$
S4:	$q3 \leftarrow x3;$
S5:	$q4 \leftarrow x4;$
S6:	$q5 \leftarrow x5;$
S7:	$q6 \leftarrow x6;$
S8:	$q7 \leftarrow x7;$ $stop = 1;$

III. Datapath Unit (DU) Design

a. Functional Block Diagram

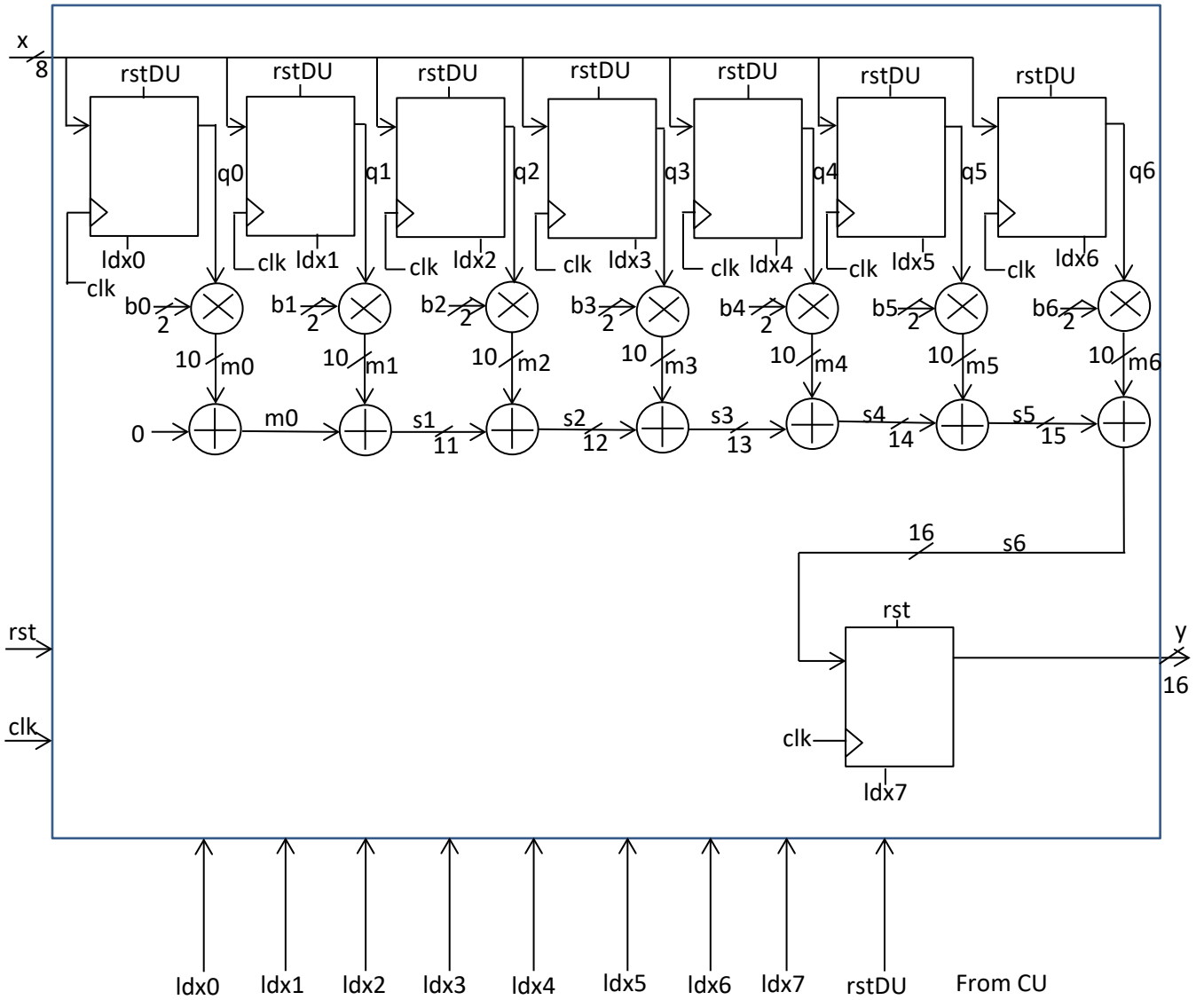

b. Verilog HDL Coding

• DU Coding

```
module DU (clk,rst,rstDU,x,y,ldx0,ldx1,ldx2,ldx3,ldx4,ldx5,ldx6,ldx7);
    input clk,rst,rstDU,ldx0,ldx1,ldx2,ldx3,ldx4,ldx5,ldx6,ldx7;
    input [7:0] x;
    output [15:0] y;
    parameter [1:0] b0=2,b1=1,b2=3,b3=1,b4=2,b5=3,b6=1; //Comment1
    wire [9:0] m0,m1,m2,m3,m4,m5,m6;
    wire [10:0] s1; wire [11:0] s2; wire [12:0] s3; wire [13:0] s4; wire [14:0] s5;
    wire [15:0] s6;
    wire [7:0] q0,q1,q2,q3,q4,q5,q6;

    reg8 regx0(x,ldx0,~clk,0,rstDU,q0); //Comment2
    assign m0=b0*q0;

    reg8 regx1(x,ldx1,~clk,0,rstDU,q1);
    assign m1=b1*q1;
    RCA16 RCAx1(0,m0,m1,s1[10],s1[9:0]);

    reg8 regx2(x,ldx2,~clk,0,rstDU,q2);
    assign m2=b2*q2;
    RCA16 RCAx2(s1[10],s1[9:0],m2,s2[11],s2[10:0]);

    reg8 regx3(x,ldx3,~clk,0,rstDU,q3);
    assign m3=b3*q3;
    RCA16 RCAx3(s2[11],s2[10:0],m3,s3[12],s3[11:0]);

    reg8 regx4(x,ldx4,~clk,0,rstDU,q4);
    assign m4=b4*q4;
    RCA16 RCAx4(s3[12],s3[11:0],m4,s4[13],s4[12:0]);

    reg8 regx5(x,ldx5,~clk,0,rstDU,q5);
    assign m5=b5*q5;
    RCA16 RCAx5(s4[13],s4[12:0],m5,s5[14],s5[13:0]);

    reg8 regx6(x,ldx6,~clk,0,rstDU,q6);
    assign m6=b6*q6;
    RCA16 RCAx6(s5[14],s5[13:0],m6,s6[15],s6[14:0]);

    reg16 regx7(s6,ldx7,~clk,0,rst,y);
endmodule
```

Discussion

Comment1:

The coefficient b is set to have 2-bit value which can take decimals of 0 to 3 in order to fulfill the requirement to get 16 bits of y value. In this case, the coefficients $b[n] = \{2\ 1\ 3\ 1\ 2\ 3\ 1\}$.

Comment2:

The clock for Datapath unit is set to be negative-edged to satisfy the setup time and the hold time.

- 8-bit Register Coding

```
module reg8 (d,en,clk,pst,rst,q);
    input [7:0] d;
    input en,clk,pst,rst;
    output [7:0] q;
    reg [7:0] q;

    always@(posedge clk or posedge pst or posedge rst)
        if (rst) q<=0;
        else if (pst) q<=1;
        else if (en) q<=d;
        else q<=q;
endmodule
```

- 16-bit Ripple Carry Adder Coding

```
module RCA16(Cin,x,y,Cout,Sum);
    input Cin;
    input [15:0] x,y;
    output [15:0] Sum;
    output Cout;
    wire [16:0] c;

    assign c[0]=Cin;
    FA u0(c[0],x[0],y[0],Sum[0],c[1]);
    FA u1(c[1],x[1],y[1],Sum[1],c[2]);
    FA u2(c[2],x[2],y[2],Sum[2],c[3]);
    FA u3(c[3],x[3],y[3],Sum[3],c[4]);
    FA u4(c[4],x[4],y[4],Sum[4],c[5]);
    FA u5(c[5],x[5],y[5],Sum[5],c[6]);
    FA u6(c[6],x[6],y[6],Sum[6],c[7]);
    FA u7(c[7],x[7],y[7],Sum[7],c[8]);
    FA u8(c[8],x[8],y[8],Sum[8],c[9]);
    FA u9(c[9],x[9],y[9],Sum[9],c[10]);
    FA u10(c[10],x[10],y[10],Sum[10],c[11]);
    FA u11(c[11],x[11],y[11],Sum[11],c[12]);
    FA u12(c[12],x[12],y[12],Sum[12],c[13]);
    FA u13(c[13],x[13],y[13],Sum[13],c[14]);
    FA u14(c[14],x[14],y[14],Sum[14],c[15]);
    FA u15(c[15],x[15],y[15],Sum[15],c[16]);
    assign Cout=c[16];

endmodule
```

- 16-bit Register Coding

```
module reg16 (d,en,clk,pst,rst,q);
    input [15:0] d;
    input en,clk,pst,rst;
    output [15:0] q;
```

```

reg [15:0] q;

always@(posedge clk or posedge pst or posedge rst)
    if (rst) q<=0;
    else if (pst) q<=1;
    else if (en) q<=d;
    else q<=q;
endmodule


```

IV. Control Unit (CU) Design

a. RTL-CS Table

State	Control Signal									
	ldx0	ldx1	ldx2	ldx3	ldx4	ldx5	ldx6	ldx7	rstDU	stop
Idle if (start), goto S1 if (!start), goto Idle	0	0	0	0	0	0	0	0	1	0
S1 goto S2	1	0	0	0	0	0	0	0	0	0
S2 goto S3	0	1	0	0	0	0	0	0	0	0
S3 goto S4	0	0	1	0	0	0	0	0	0	0
S4 goto S5	0	0	0	1	0	0	0	0	0	0
S5 goto S6	0	0	0	0	1	0	0	0	0	0
S6 goto S7	0	0	0	0	0	1	0	0	0	0
S7 goto S8	0	0	0	0	0	0	1	0	0	0
S8 goto Idle	0	0	0	0	0	0	0	1	0	1

b. Functional Block Diagram

 

c. Verilog HDL Coding

```
module CU (start,rst,clk,ldx0,ldx1,ldx2,ldx3,ldx4,ldx5,ldx6,ldx7,rstDU,stop);
    input start,rst,clk;
    output ldx0,ldx1,ldx2,ldx3,ldx4,ldx5,ldx6,ldx7,rstDU,stop;
    parameter [3:0] s0=0,s1=1,s2=2,s3=3,s4=4,s5=5,s6=6,s7=7,s8=8;
    reg [3:0] PS,NS;
    reg [9:0] Control;


    //state reg
    always@(posedge clk or posedge rst) begin
        if (rst) PS<=0;
        else PS<=NS; end

    //NS and output logic
    always@(PS or start) begin
        Control=0;
        case (PS)
            s0: begin NS=start? s1:s0; Control=10'b00000000010; end
            s1: begin NS=s2; Control=10'b1000000000; end
            s2: begin NS=s3; Control=10'b0100000000; end
            s3: begin NS=s4; Control=10'b0010000000; end
            s4: begin NS=s5; Control=10'b0001000000; end
            s5: begin NS=s6; Control=10'b0000100000; end
            s6: begin NS=s7; Control=10'b0000010000; end
            s7: begin NS=s8; Control=10'b0000001000; end
            s8: begin NS=s0; Control=10'b0000000101; end
        endcase
    end

    assign {ldx0,ldx1,ldx2,ldx3,ldx4,ldx5,ldx6,ldx7,rstDU,stop}=Control;
endmodule
```

V. CU-DU Integration

a. Top-Level Functional Block Diagram

 

b. Top-Level Verilog HDL Coding

```
module SevenTapFIRFilter(start,rst,clk,stop,x,y);
    input start,rst,clk;
    input [7:0] x;
    output stop;
    output [15:0] y;
    wire w0,w1,w2,w3,w4,w5,w6,w7;

    CU u0(start,rst,clk,w0,w1,w2,w3,w4,w5,w6,w7,rstDU,stop);
    DU u1(clk,rst,rstDU,x,y,w0,w1,w2,w3,w4,w5,w6,w7);

endmodule
```

i. Design Simulation
a. Datapath Unit (DU)

 


Figure 2: DU Waveform.

Discussion:

The input is set to be $x[n] = \{3\ 4\ 5\ 6\ 7\ 9\ 12\}$. The expected output is $y[n] = 84$. Thus, the waveform matches the output.

b. Control Unit (CU)

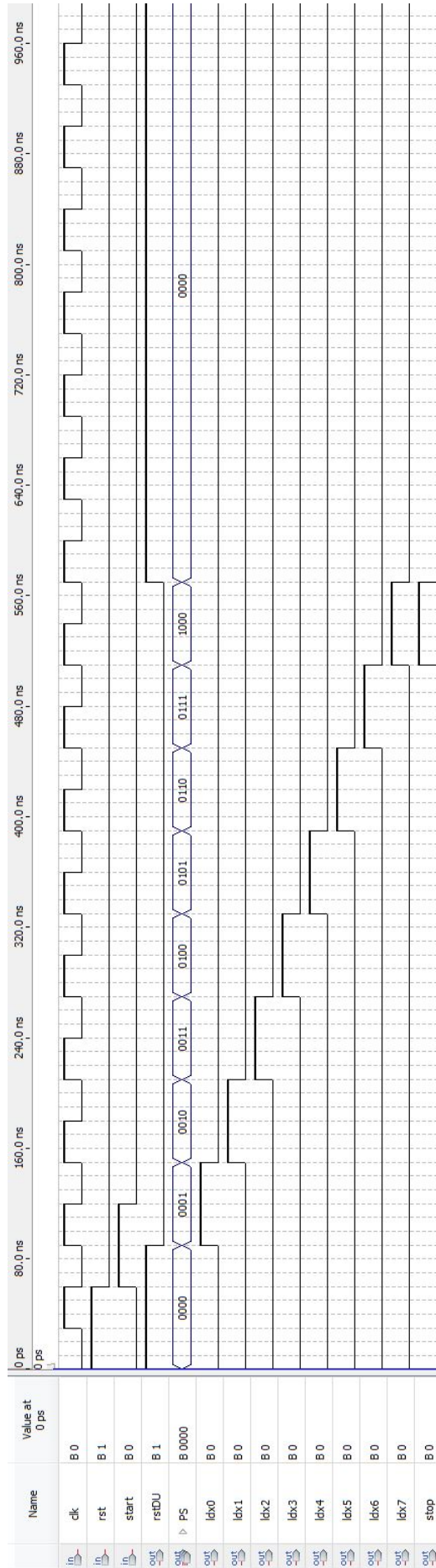


Figure 3: CU Waveform with Present State (PS) shown.

c. CU-DU Integration

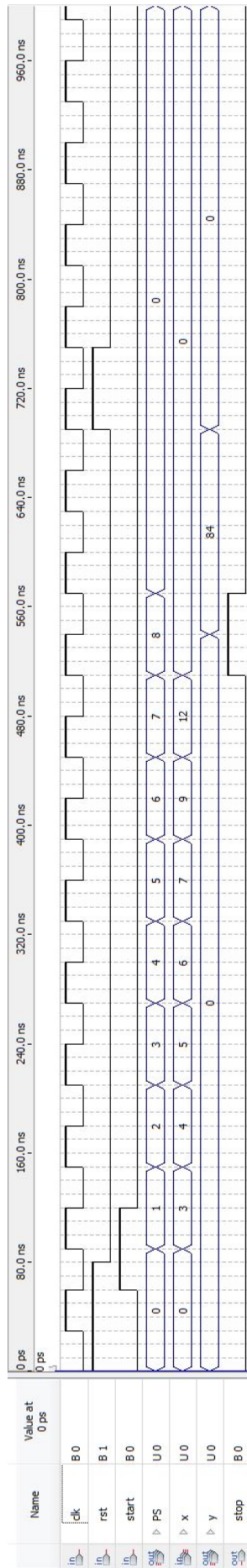


Figure 4: The Top-level Waveform for 7-tap FIR filter.

DISCUSSION

The coefficient we set is $b[n] = \{2\ 1\ 3\ 1\ 2\ 3\ 1\}$. The coefficient b is set to have 2-bit value which can take decimals of 0 to 3 in order to fulfill the requirement to get 16 bits of y value. The input is set to be $x[n] = \{3\ 4\ 5\ 6\ 7\ 9\ 12\}$. The expected output is $y[n] = 84$. Thus, the waveform matches the output.

The clock for Datapath unit is set to be negative-edged to satisfy the setup time and the hold time.

CONCLUSION

The output matches the calculation where the $b[n] = \{2\ 1\ 3\ 1\ 2\ 3\ 1\}$ and $x[n] = \{3\ 4\ 5\ 6\ 7\ 9\ 12\}$ would get $y[n] = 84$. A 7-tap FIR filter is successfully designed.